

P.O.Box 845-50400 Busia(K)
principal@auc.ac.ke
Tel: +254 741 217 185
+254 736 044 469
off Busia-Malaba road

OFFICE OF THE DEPUTY PRINCIPAL
ACADEMICS, STUDENT AFFAIRS AND RESEARCH

UNIVERSITY EXAMINATIONS

2018/2019 ACADEMIC YEAR

SECOND YEAR FIRST SEMESTER REGULAR EXAMINATION

**FOR THE DEGREE OF BACHELOR OF
COMPUTER SCIENCE**

COURSE CODE: COM 215

COURSE TITLE: ELECTRICAL CIRCUITS

DATE: 13TH DECEMBER, 2018

TIME: 9.00 AM – 12.00 NOON

INSTRUCTION TO CANDIDATES

- SEE INSIDE

THIS PAPER CONSISTS OF 5 PRINTED PAGES

PLEASE TURN OVER

INSTRUCTIONS TO CANDIDATES

- Answer **ALL** Questions from section A and any other **THREE** questions.
- Maps and diagrams should be used whenever they serve to illustrate the answer
- Do not write on the question paper

SECTION A (24 MARKS) COMPULSORY**QUESTION ONE (12 Marks)**

- Find the total charge in a cylindrical conductor (solid wire) and compute the current flowing in the wire. 5 Marks
- State Kirchhoff's voltage and current laws. 3 Marks
- Apply both KVL and KCL to each of the two circuits depicted in Figure 1a & 1b below to obtain equations for each of the two circuits by applying KCL and KVL. 8 Marks

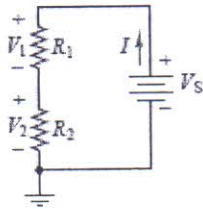


Fig. 1a

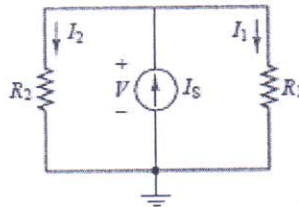


Fig. 1b

- Determine the voltage v_3 in the circuit of Figure 2. 4 Marks

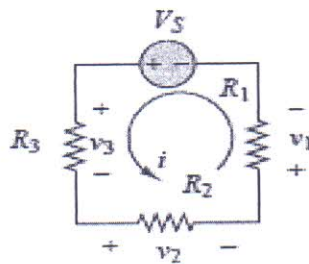


Fig. 2

QUESTION TWO (12 Marks)


- State Superposition theorem. (3 Marks)
- A 200 V, 50 Hz, inductive circuit takes a current of 10A, lagging 30 degree.
Find
(i) the resistance

- (ii) reactance
 (iii) inductance of the coil. (9 Marks)

SECTION B (36 MARKS)

QUESTION THREE (12 Marks)

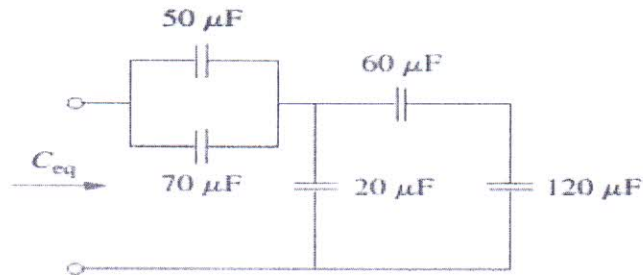
- a. Find C_{eq} in figure below. Clearly show your working and reasoning. (6 Marks)



- b. A resistance R , an inductance $L=0.01$ H and a capacitance C are connected in series. When an alternating voltage $v=400\sin(3000t-20^\circ)$ is applied to the series combination, the current flowing is $10.2\sin(3000t-65^\circ)$. Find the values of R and C . (6 Marks)

QUESTION FOUR (12 Marks)

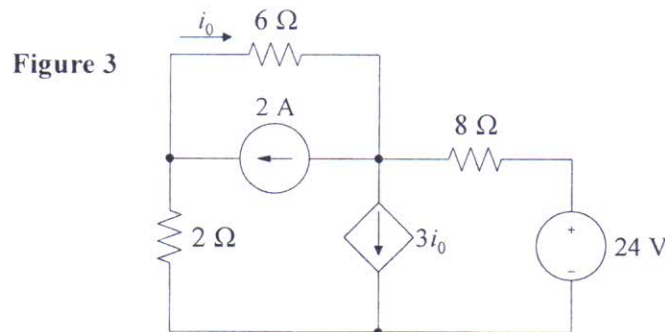
- a) Use superposition to find the current i_0 in the circuit in Figure 3. (6Marks)




- b) Obtain the Thevenin equivalent of the circuit in Figure 5 with respect to the terminals a-b.

(6Marks)

Figure 5

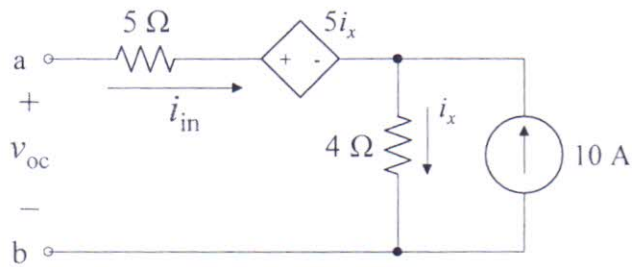**QUESTION FIVE (12 Marks)**

- A wire carries a steady current of 0.1 A over a period of 20 s. What total charge passes through the wire in this time interval? (4 Marks)
- A metallic conductor has a resistivity of $18 \times 10^{-6} \Omega \cdot \text{m}$. What is the resistance of a piece that is 30 m long and has a uniform cross-sectional area of 3.0 mm^2 ? (4 Marks)
- If $R_1 = R_2 = R_3 = R_4 = 10 \Omega$ and $R = 20 \Omega$, what is the equivalent resistor of the circuit? (4 Marks)

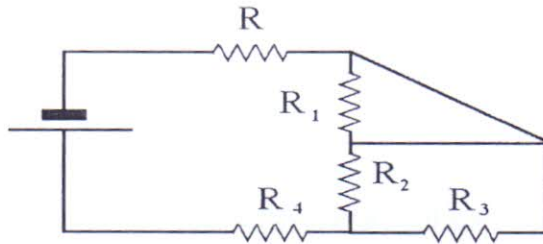**QUESTION SIX (12 Marks)**

- State Thevenin's theorem and by use of diagram(s), explain its application in electrical circuits analysis. (3 Marks)
- From first principles, prove that in a series circuit for three resistors R_1 , R_2 , and R_3 , the effective resistance (R_{eff}) is given by $R_{\text{eff}} = R_1 + R_2 + R_3$ (3 Marks)
- Define Laplace transform of a function $f(t)$; hence find the Laplace transforms for the function (3 Marks)
- Explain the operation of a series circuit. (3 Marks)

QUESTION SEVEN (12 Marks)

- State Norton's theorem and by use of an appropriate diagram explain its application in electrical circuit analysis. (4 Marks)
- Define the following terms as applied in electrical principles circuitries: (4 Marks)



- i. Impedance
 - ii. Resonance
 - iii. Reactance
 - iv. Conductance
- c. Explain the operation of a parallel circuit, hence from first principles prove that in a parallel circuit for the three resistors R_1 , R_2 , and R_3 , the resistance (R_{eff}) is given by $R_{eff} = R_1R_2R_3/(R_1R_2+R_2R_3+R_3R_1)$ (4 Marks)

